
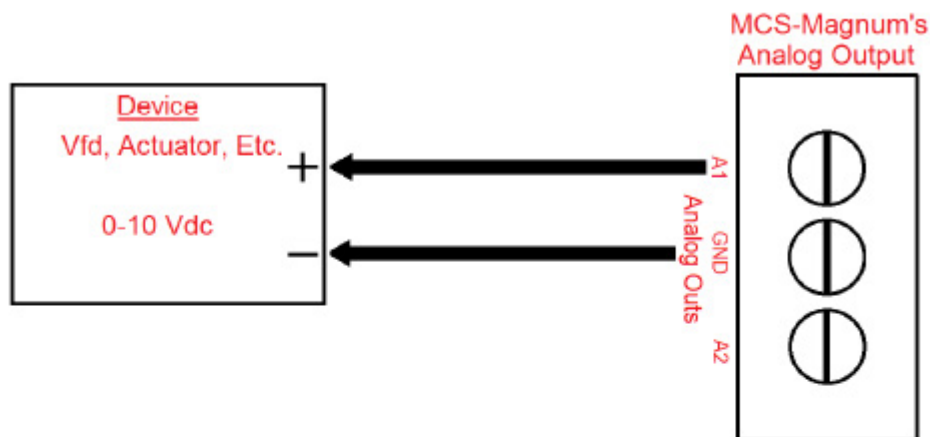


How to Convert a 0-10Vdc Analog Output to 4-20mA

Typicaly 0-10Vdc output:

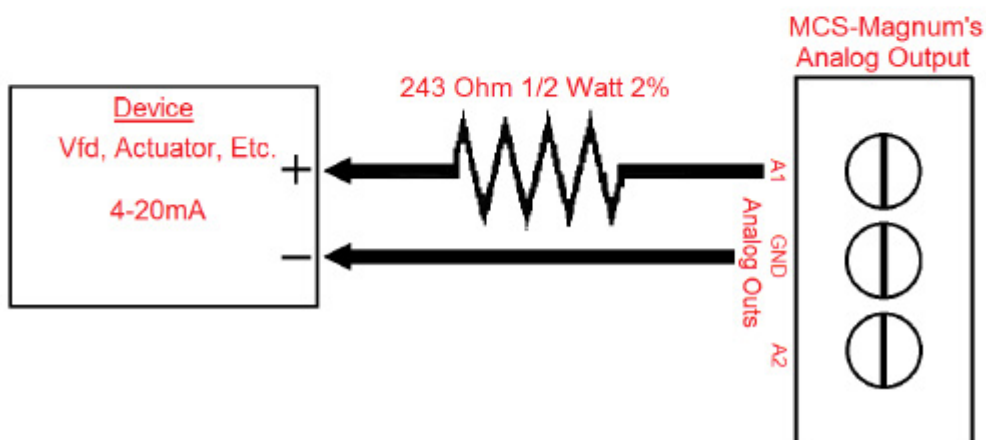

Conversion 4-20mA output:



Any questions regarding this release, contact: support@mcscontrols.com

Information contained in this document has been prepared by Micro Control Systems, Inc. and is copyright © protected 2025. Copying or distributing this document is prohibited unless expressly approved by MCS.

Release - 2025-09-17